

# Py 202

exam: max 95

top 1/4 85

median 80

3/4 quartile 72.5

min 54



ex




$V(\text{at center}) = V(r=a)$  4 points!

$$V = - \int_{\infty}^{r=a} \vec{E} \cdot d\vec{r} \quad 4 \text{ points!}$$

## Quiz (clicker)

1)

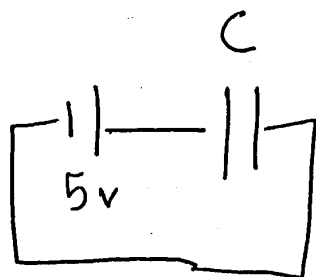


Q's?

$$C = \frac{Q}{V}$$

$$Q = CV$$

$$Q_1 = CV_1$$

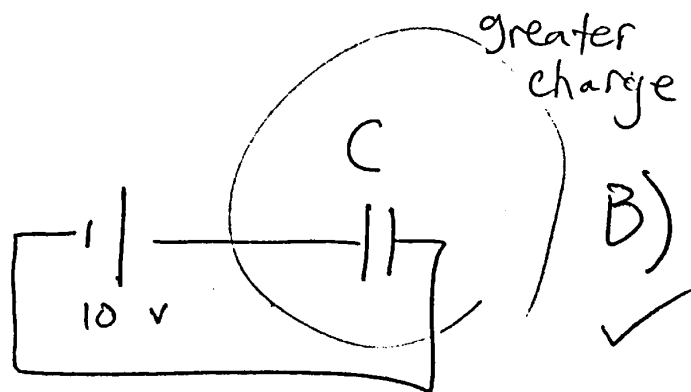


$$V_1 \leq V$$



$$Q_2$$

$$Q_2 = CV_2$$

1)

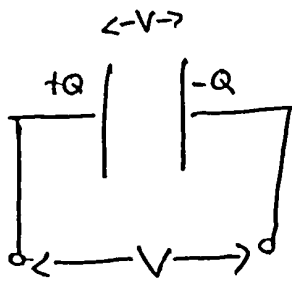

2)

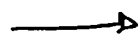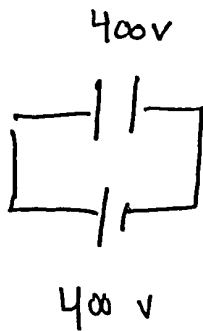

Area A

distance d

I don't know capacitance as function of A and d!

but, it's something over d: Same area

$$C = \frac{k}{2d} \rightarrow \frac{k}{2d}$$

$$\Delta C \rightarrow \frac{1}{2} C$$

$$\Delta V = \frac{Q}{C} \rightarrow \frac{1}{2} C, 2 \times V$$

$$V = 800 \text{ V}$$

D) ✓

C, V known

$$Q = CV = C(400 \text{ V}) = Q_{\text{old}}$$

(disconnected)  $\Delta Q$  stays same. C, V will change.  $\Delta C = \frac{\epsilon_0 A}{d} \rightarrow$  basically what I said.

Quiz takeaway:  $C = \frac{\epsilon_0 A}{d}$

$$C = \frac{Q}{V}$$

Capacitance =  $\frac{\text{charge on capacitor}}{\text{potential difference across capacitor}}$

↑  
Property  
of  
device

potential difference across capacitor


$C_{eq}$  Derivation Method

Connecting Capacitors

$$Q_{tot} = Q_1 + Q_2 = C_1 V + C_2 V = V(C_1 + C_2)$$

$$Q = C_{eq} V$$

Parallel

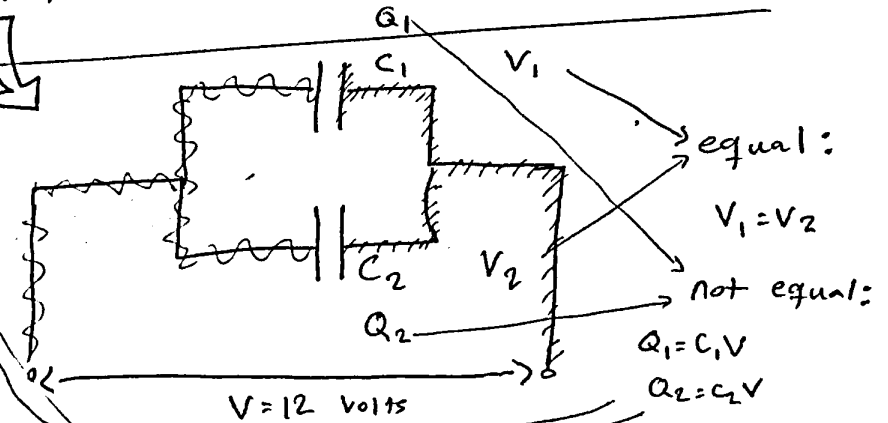

equal:

$$V_1 = V_2$$

not equal:

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$


anything connected by conducting wire (or wires) is at same potential

in parallel:  $C_{eq} = C_1 + C_2$

$$V_1 + V_2 = 12 \text{ volts} = V_{tot}$$


$$\frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V_{tot}$$
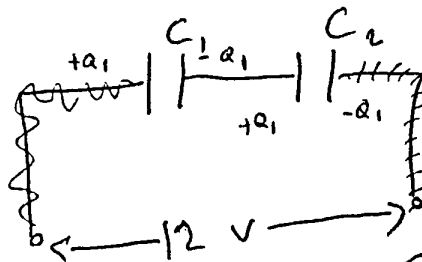
$$Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{Q}{C_{eq}} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$




Series

ex

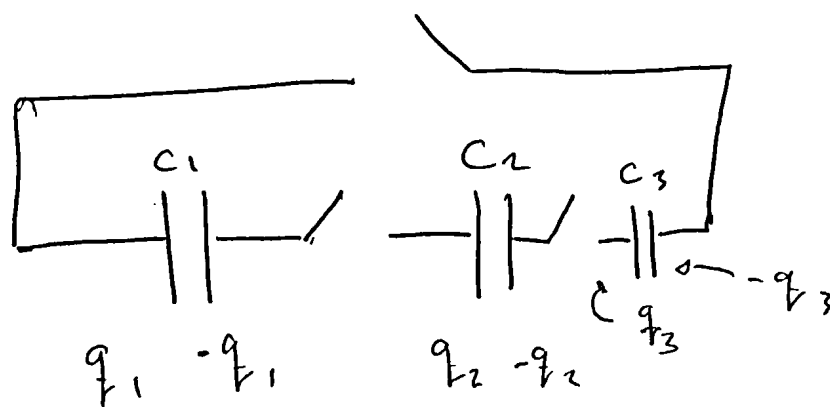


$$V_1 = V_2 = V_3$$

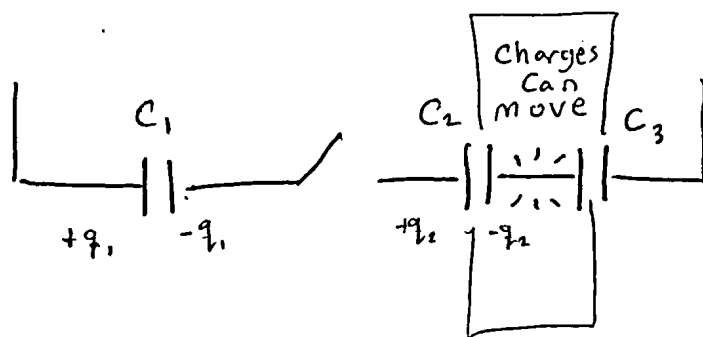


$$V_1 = V_2 = V_3$$




ex

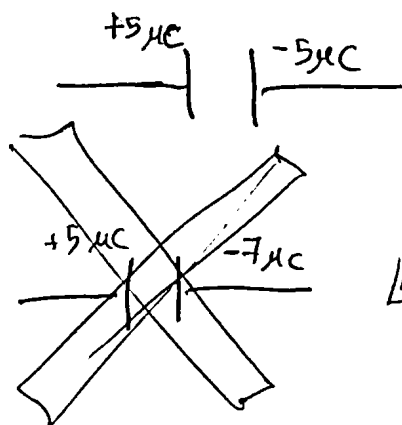

Not A Capacitor!

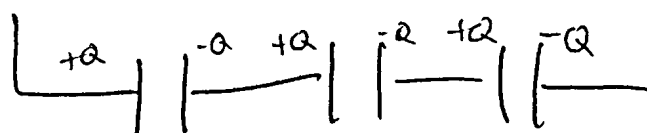


ex

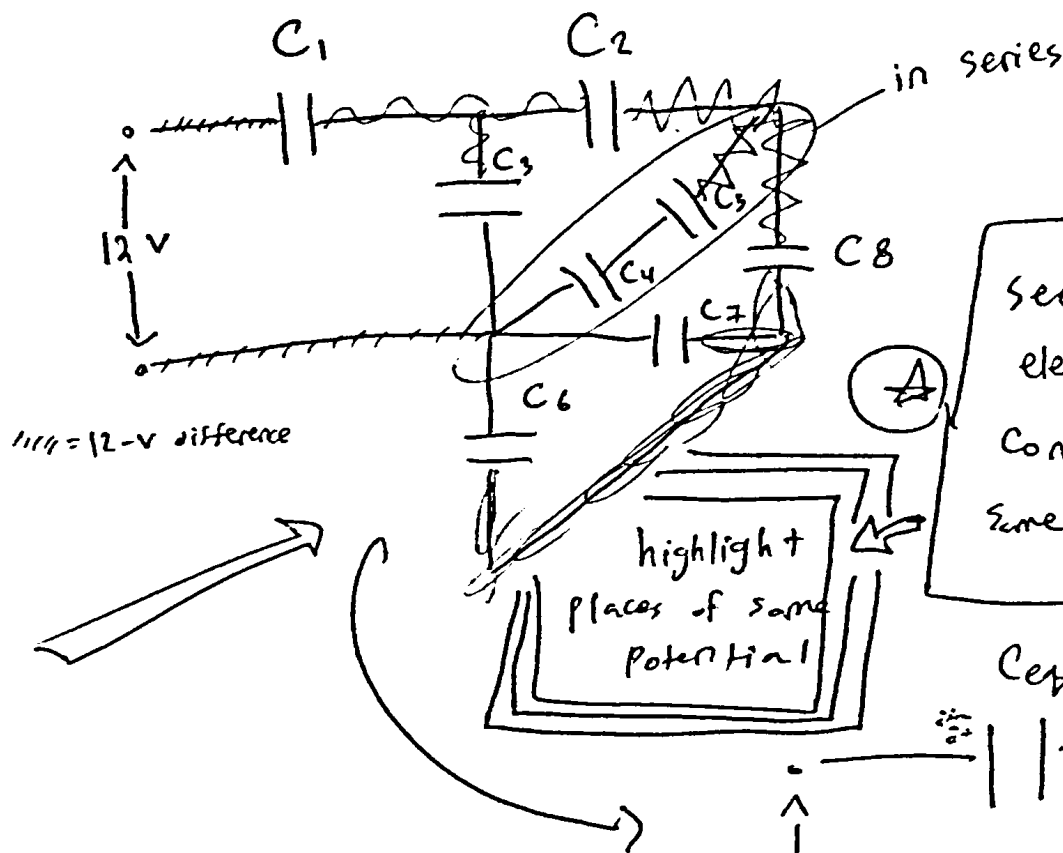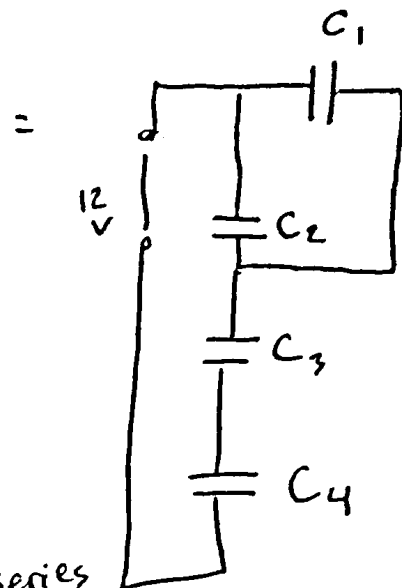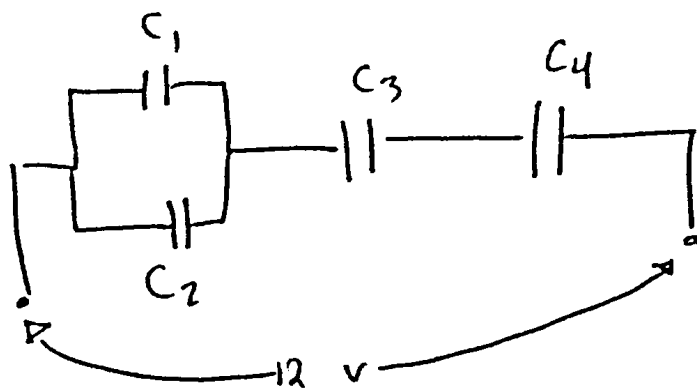

See which elements are connected by same wire!

highlight + places of same potential

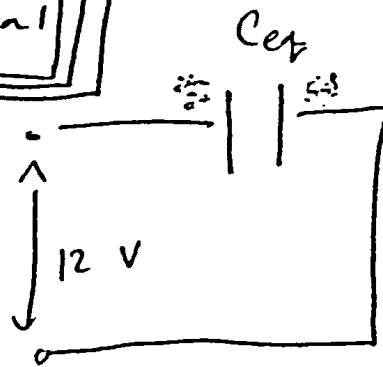

given  $Q$ , find  $C_{eq}$

- Demos