

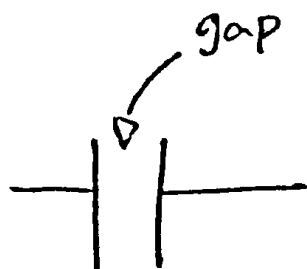
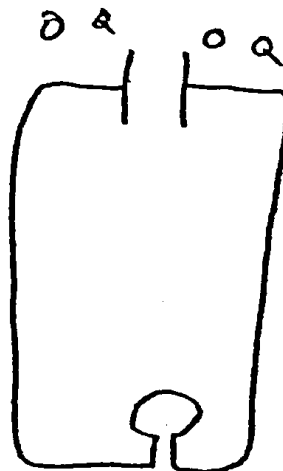
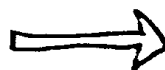
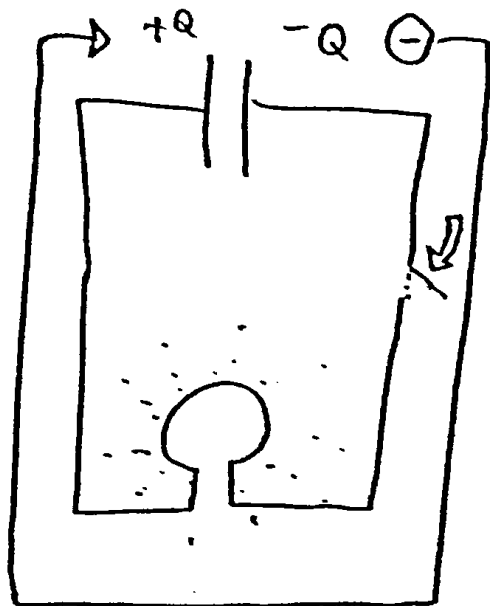


$$C = \frac{Q}{V_{gap}}$$


PY 202

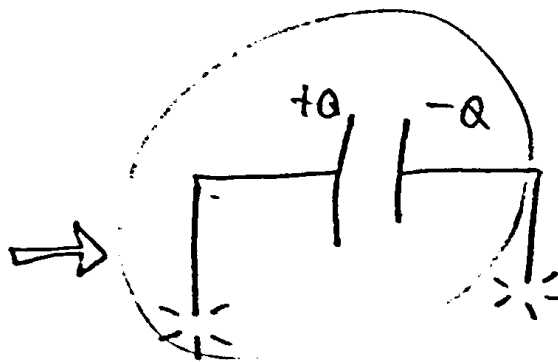

Charge
Dynamics
w/
Capacitors

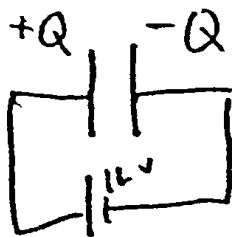


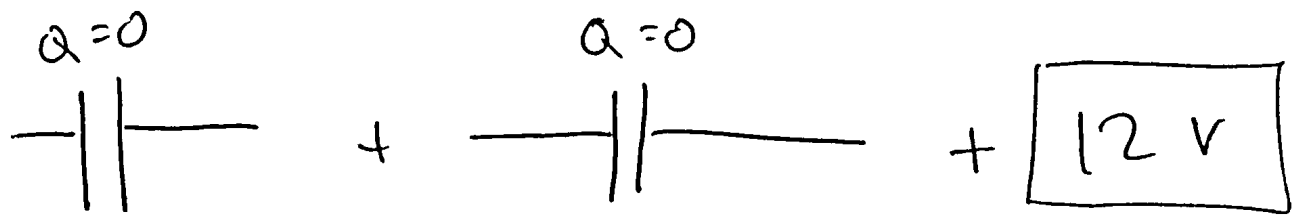Unlike
batteries,
capacitors
don't provide
charge for
a long
time.




in series


①

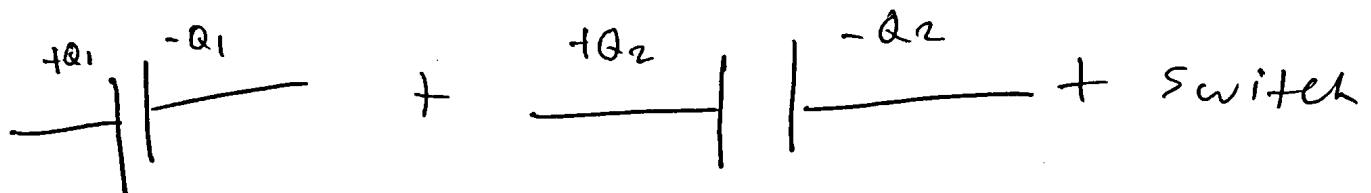

②

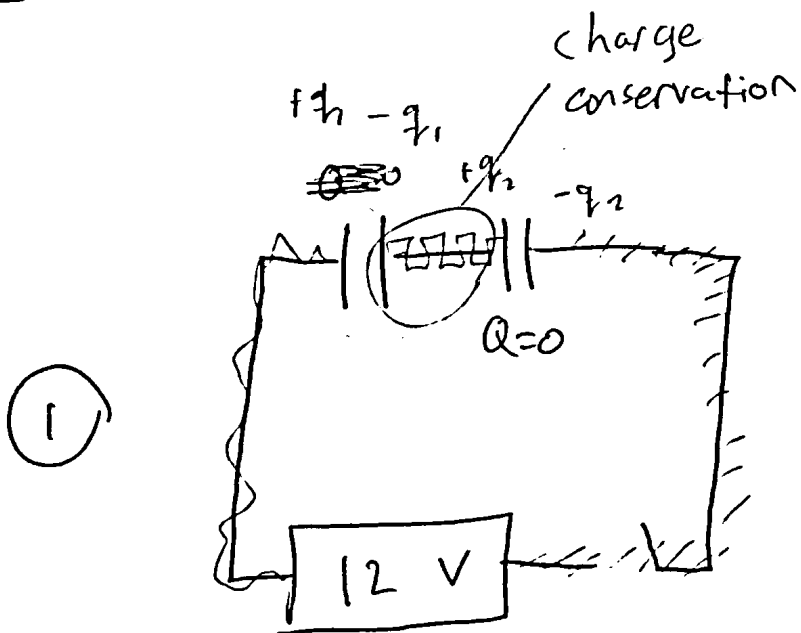

②

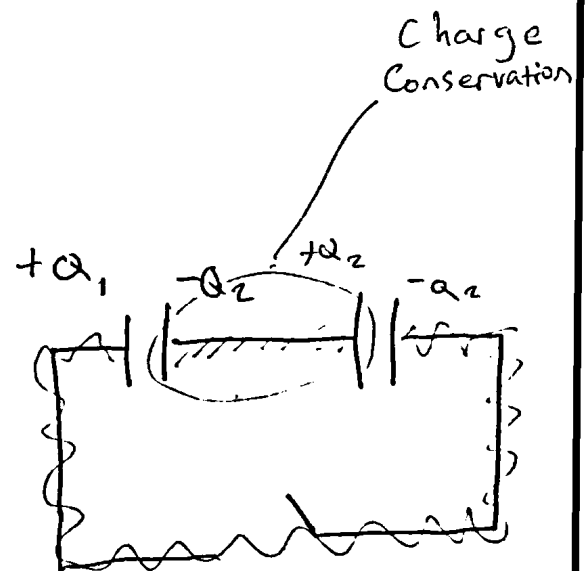


$$V_1 + V_2 = 0$$

$$V_1 + V_2 = 12\text{ V}$$


Charge conservation: $-Q_1 + Q_2 = -q_1 + q_2$

(2)

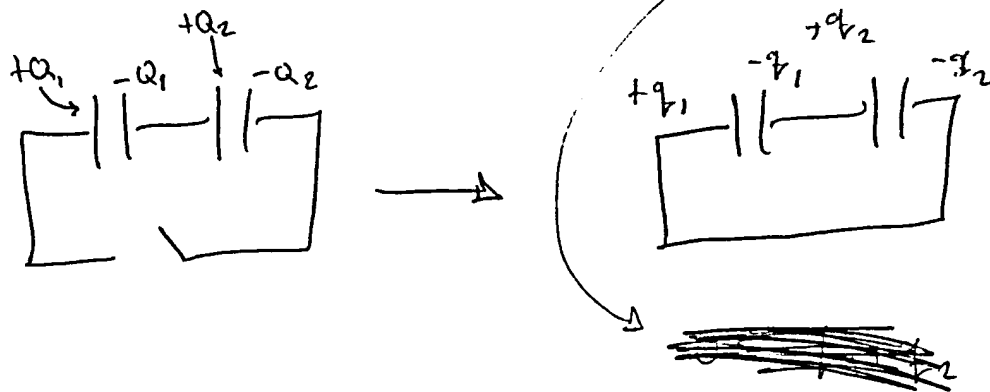

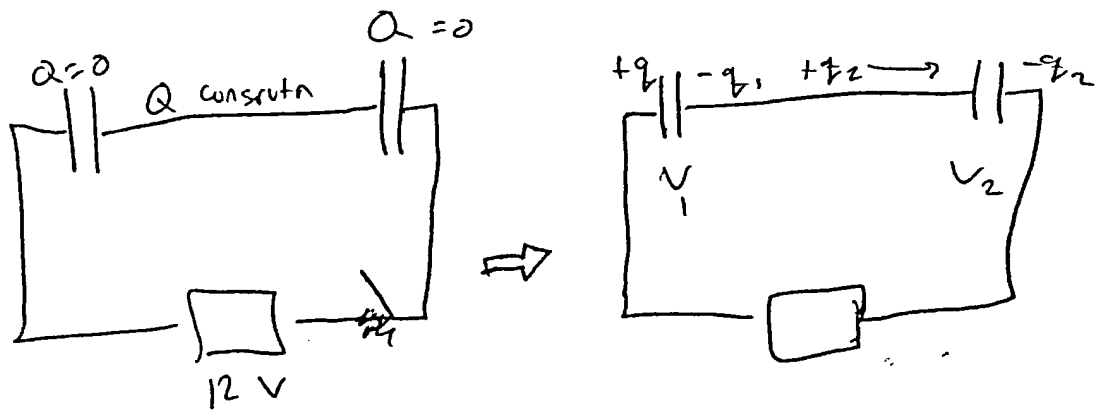(3)

Charge conservation: ~~$-Q_1 + Q_2$~~ $= -q_1 + q_2$





$$0 = -q_1 + q_2$$


→ equal charge

But

$$V_1 \neq V_2$$

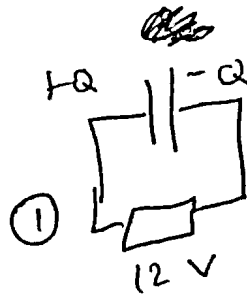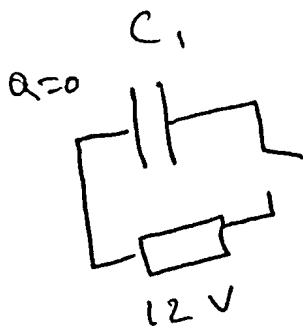

$Ac_1: A$
 $dc_1: d$

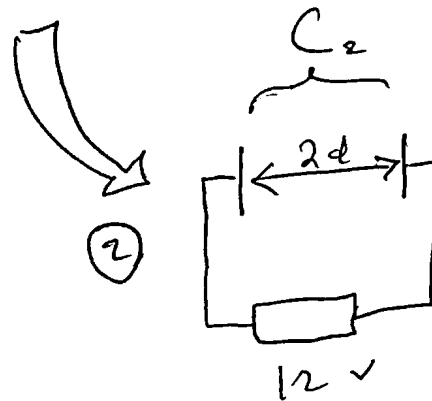

"d" = $1d$

$$C_1 = \frac{\epsilon_0 A}{d}$$

$$V_1 = 12$$

Q_1

①


$2d$:

$$C_2 = \frac{\epsilon_0 A}{2d}$$

$$V_2 = 12 \text{ V}$$

Q_2


②

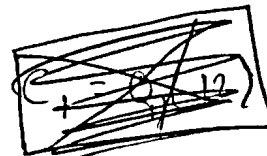

$$Q = CV$$

$$Q_1 = C_1(12)$$

$$Q_1 = C_1(12)$$

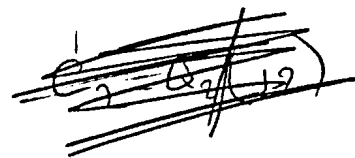

$$Q_2 = C_2(12)$$

$$Q_2 = C_1(6)$$

$$Q_2 = \frac{Q_1}{2}$$

quiz

$$E = -\vec{\nabla} V$$

So, where slope V is max.

(B) ✓

$$C = \frac{\epsilon_0 A}{d} = \frac{ab\epsilon_0}{d} = \epsilon_0 \left(\frac{ab}{d} \right)$$

$$\epsilon_0 \frac{(2)^2 ab}{2d} = 2 \left(\frac{ab}{d} \right)$$

doubles: (B) ✓

$$C_{\max} = 2C$$

$$C_{\min} = \frac{C^2}{2C} = \frac{C}{2}$$

$$\frac{2C}{C/2} = 4$$

$$C_{\max} = 4 C_{\min} \quad (A) \checkmark$$

$$\gamma_{ws} = \gamma_{ws}^0 - \frac{CV^2}{2} = \gamma_{ws}^0 - \frac{\epsilon_r \epsilon_0 V^2}{2t}$$

→ fluoropolymers
→ Patterning

Surface tension/energy?

$$\gamma_{ws} = \gamma_s - \gamma_w \cos(\theta)$$

$$\cos \theta = \left(\frac{\gamma_s - \gamma_{ws}^0 + \frac{CV^2}{2}}{\gamma_w} \right)$$

① FluoroPel
(super-)hydrophobic V-Series

② CYTOP

③ Teflon AF

↳ or EWOLF

electrowetting

microfluidics (droplet-based)

microdroplets: droplet generation
motion
sorting
merging
breakup

air



dielectric
 $\epsilon_r > 1$



less charge on electroscope



more charge on capacitor

$$C_{air} = C_0$$


$$C_{air} = \frac{Q_{air}}{V_{air}}$$

$$C_{dielectric} = \epsilon_r C_0$$

$$\cancel{C_{air}} = C_{diel} = \frac{Q_{air}}{V_{diel}} = \frac{Q_{air}}{V_{air}/\epsilon_r}$$


$$C_{diel} = \epsilon_r C_{air}$$
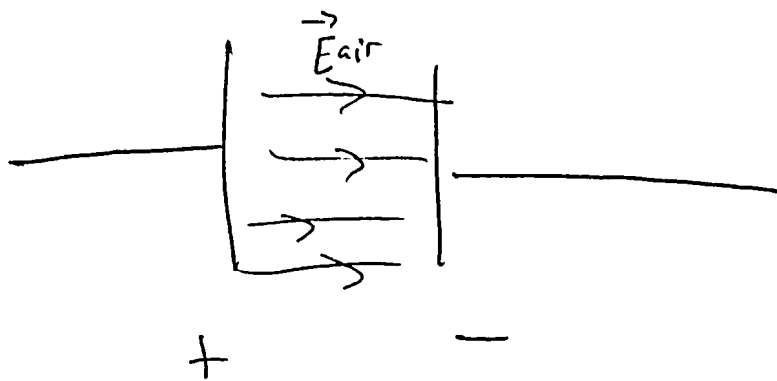
$$V_{diel} = \frac{V_{air}}{\epsilon_r}$$





$$V_{air} = -\int_0^d \vec{E} \cdot d\vec{l} = E_{air} d$$
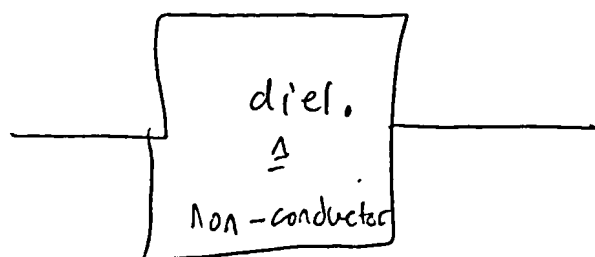
$$V_{diel} = \frac{V_{air}}{k} = \frac{E_{air} d}{k} = \left(\frac{E_{air}}{k} \right) d = E_{diel} d$$



Energy storage:

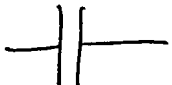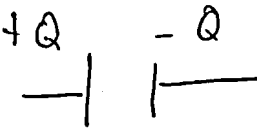go from  $Q=0$ to 

Energy Storage

$U = \frac{1}{2} \frac{Q^2}{C}$

For each charge dq added, el. potential E of

plate changes:

$dU = \frac{q}{C} dq \Rightarrow U = \int dU = \int_0^Q \frac{q}{C} dq$

$$C = \frac{Q}{V}$$


$$\Rightarrow U = \frac{1}{2} QV$$

$$Q = CV \Rightarrow$$

$$U = \frac{1}{2} CV^2$$

$$U = \frac{1}{2} \frac{Q^2}{C}$$

ex)

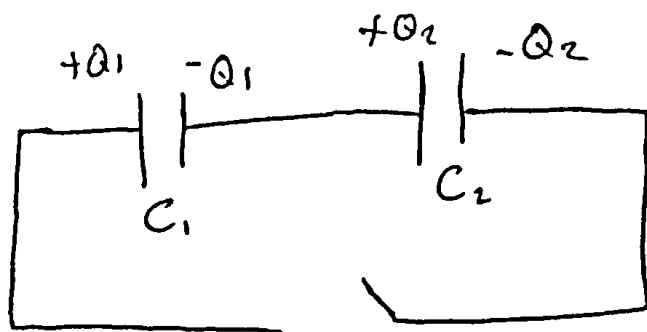

$$V_1 + V_2 = 0$$

$$V_1 = ?$$

$$V_2 = ?$$

$$U_1 = \frac{1}{2} \frac{Q_1^2}{C_1}$$

$$U_2 = \frac{1}{2} \frac{Q_2^2}{C_2}$$

→ disconnected cap: use C and Q to find U

→ connected cap: $Q = CV$, etc.