

PY 202

Wed, Feb. 15

reading: 25-6

→ midterm 2: 24, 25

Kirchhoff

(Friday: RC circuits)

(Monday: review)

HW 25


- 1) easy 2) easy 3) Kirchhoff
4) RC 5) Req, Ohm's Law*
6) Kirchhoff 7) RC ^{hard}

- resistors in parallel
- resistors in series
- P dissipated in resistor?
- Kirchhoff's Rules

} Req = ? ②

① Power

→ I

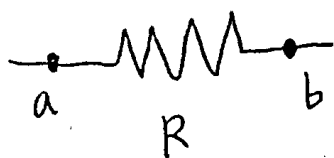

$V_a > V_b$

Move charge dq from a to b

$\Delta U = \Delta Q (V_b - V_a)$ } energy loss

rate of energy loss

$$\frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} (V_b - V_a)$$
$$= I (V_b - V_a)$$

"Charge @"


$$\frac{du}{dt} = I(V_b - V_a)$$

$$V = \Delta V = V_b - V_a$$


$$P = \frac{du}{dt} = I(V_b - V_a)$$

$$P = IV \text{ Power}$$

② Req, Series and Parallel

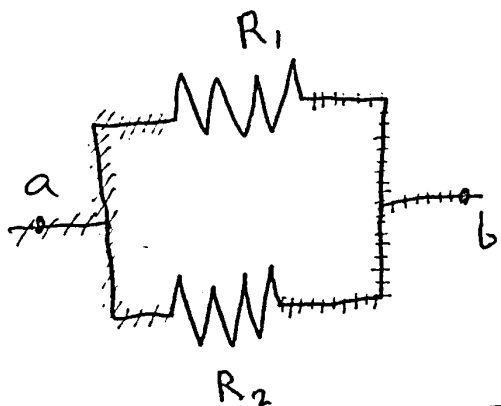

Parallel

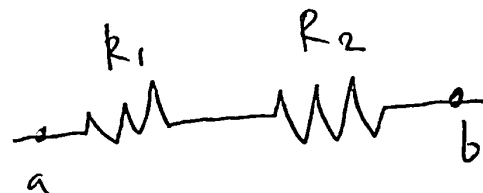

Series

$$V_{AB} = 12 \text{ volts}$$

$$V_1 = V_2 = V_{AB}$$

Ohm's Law


$$I = V/R$$

$$I = \frac{V_{AB}}{R_{eq}} = I_1 + I_2$$


$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}$$

$$I = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2} = \frac{V_{AB}}{R_{eq}} \Rightarrow \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{eq}}$$

$$I_1 + I_2 = I$$

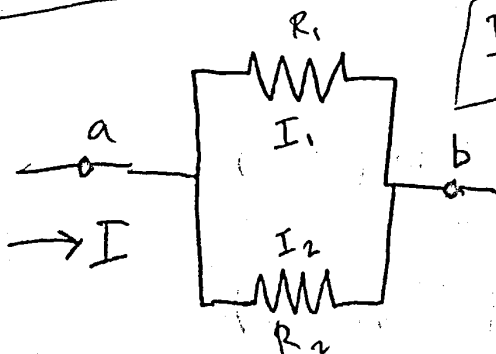

Series!

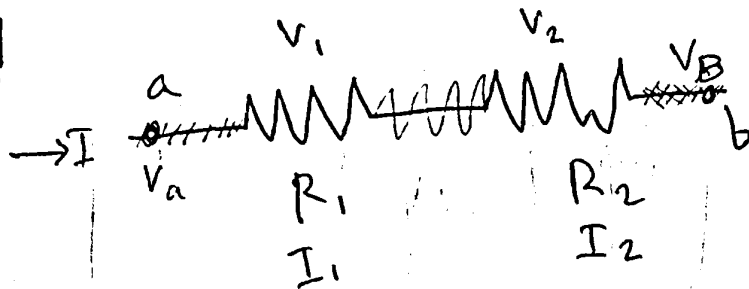

$$V_1 + V_2 = V_{ab}$$

$$I_1 = I_2 = I$$

+ Ohm's Law:

$$V_{ab} = I R_{eq}$$

$$V_{ab} = V_1 + V_2 = I R_1 + I R_2$$

$$I(R_1 + R_2) = I R_{eq}$$

$$R_{eq} = R_1 + R_2$$

$$\text{Parallel: } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

+ Ohm's Law

method: when are
voltages / currents
the same?


$$\text{Series: } R_{eq} = R_1 + R_2$$

(Caps: when are
currents / q's

the same?)

+ Cap Law

ex]

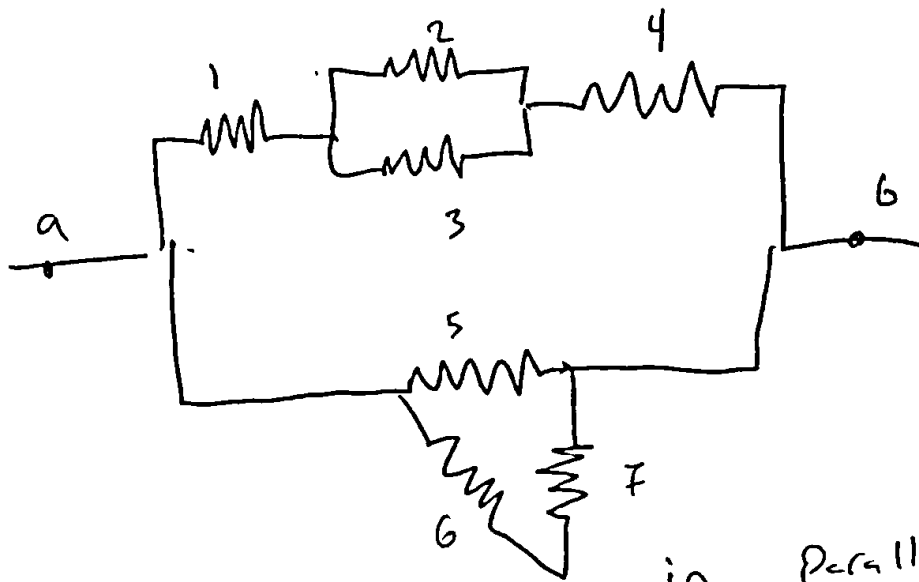

in series:

R_1, R_{23}, R_4

R_6, R_7

in parallel:

R_{1234}, R_{567}


R_5, R_{67}

R_2, R_3



③ Kirchhoff's Rules

① junction rule

② loop rule

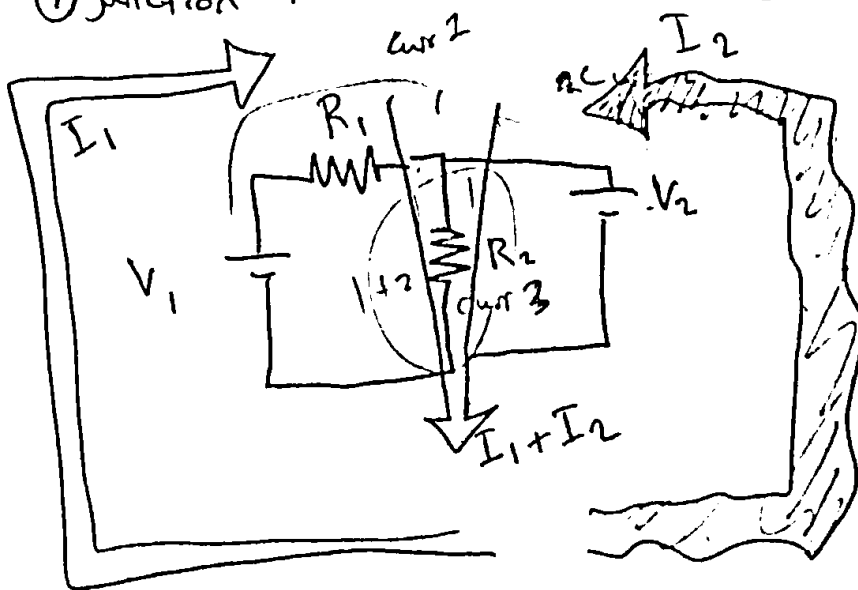

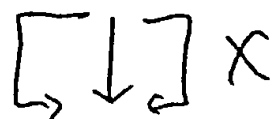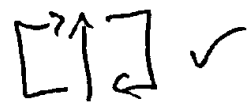Labels, directions free —
just be consistent!



① Junction Rule


$$\sum I_{\text{into junction}} = \sum I_{\text{out of junction}}$$

② (Loop Rule)

$$\sum V_i = 0$$

+ : low \rightarrow high Potential
 - : high \rightarrow low Potential



based on direction thru loop

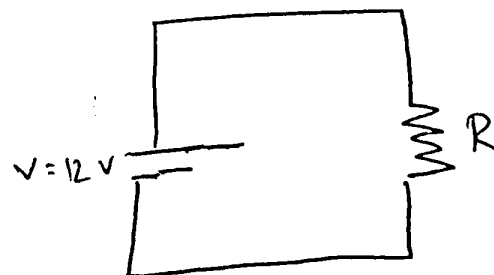

$$V_R = 12V = V$$

$$V_R - V = 0$$

identify high/low Potential sides :

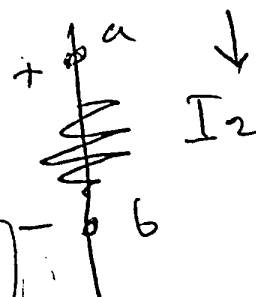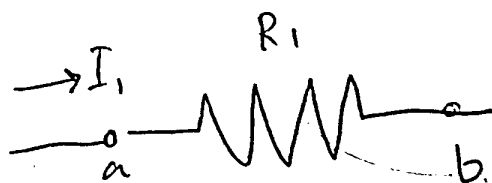

junction rule

$$I_1 = I_2 + I_3$$

Left loop (clockwise)


loop rule

$$+V_1 - I_1 R_1 - I_3 R_2 = 0$$

right loop (clockwise)

loop rule

$$-V_2 - I_2 R_3 + R_2 I_3 = 0$$

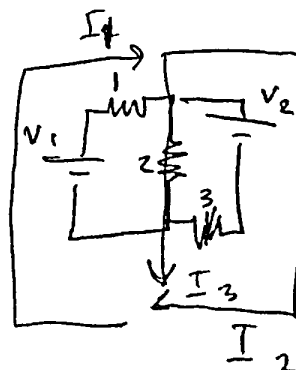

use loops and junction rule to solve for unknown currents

▷ outside loop (clockwise)

$$V_1 - I_1 R_1 - V_2 - I_2 R_3 = 0 \quad (III)$$

$$(I) + (II) = (III)$$

▷ Pick simplest loop rules (fewest terms)


▷ Kirchhoff's rules for N currents

- junction rule $\rightarrow 1$ eq.
- loop rule $\rightarrow N-1$ eq.

Get enough loop eqns. until you have enough eqns. to find all variables

- label currents
- label high and low potentials

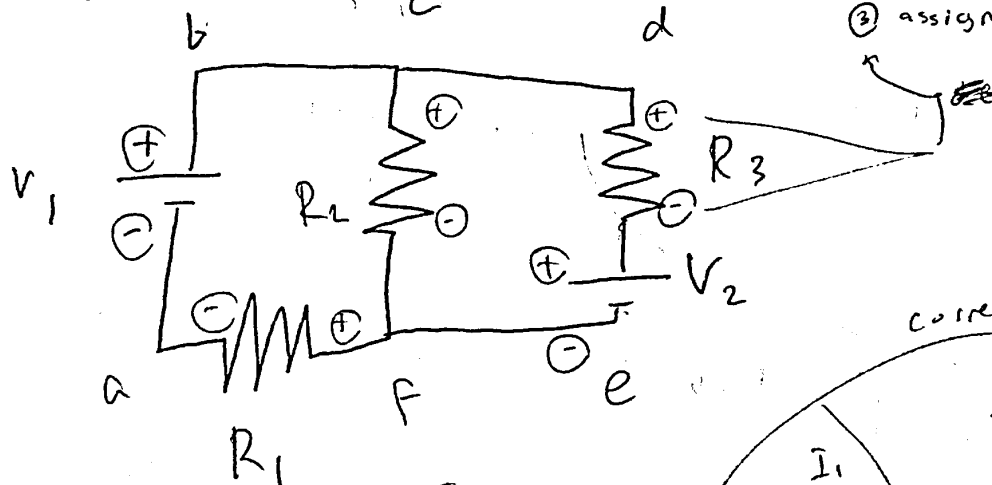- ① current directions
- ② current goes high \rightarrow low
- ③ assign V $+/-$



junction: define currents
at c: $I_1 = I_2 + I_3$
at f:

loop:

abcfa (cw): $V_1 - I_2 R_2 - R_1 I_1 = 0$
 edefc (cw): $-I_3 R_3 - V_2 + I_2 R_2 = 0$
 abcdefa (cw): $V_1 - I_3 R_3 - V_2 - I_1 R_1 = 0$

